
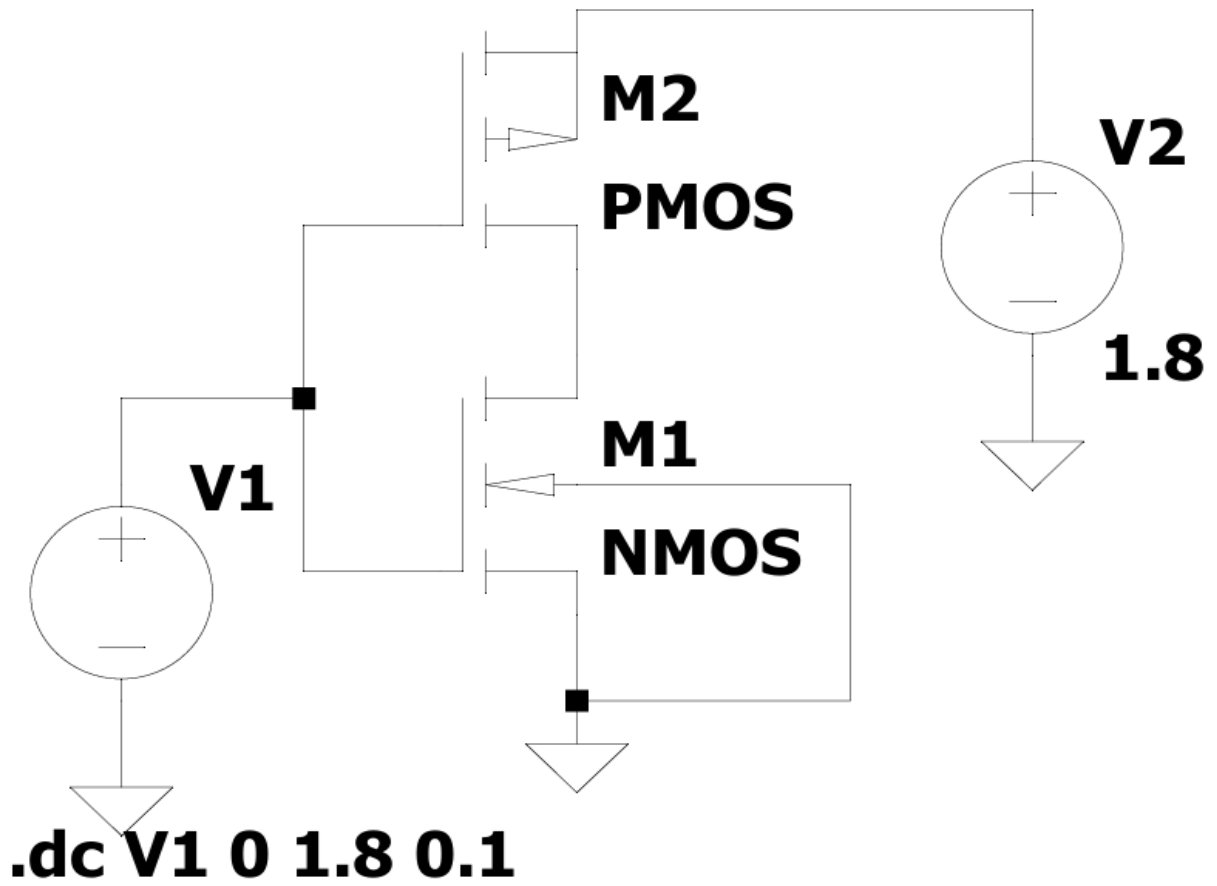


DC ANALYSIS OF CMOS INVERTER

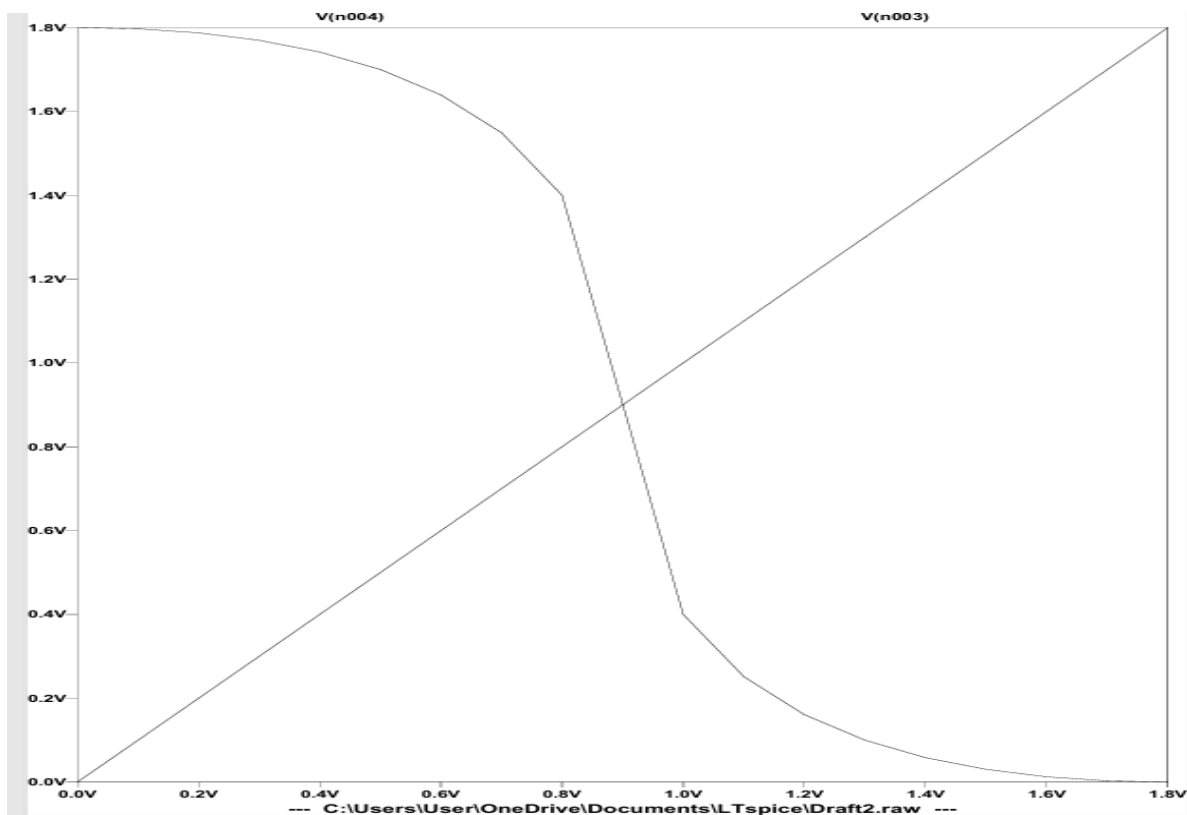
SCHEMATIC OF CMOS INVERTER SIMULATED IN LTSPICE:



OUTPUT OF CMOS INVERTER IN LTSPICE:



STICK DIAGRAM:

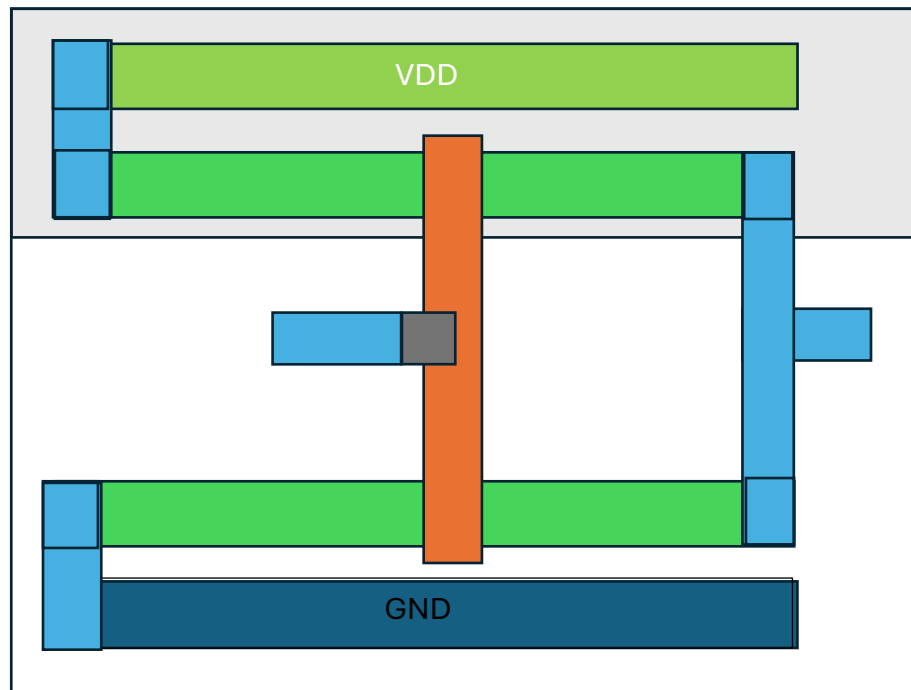

LAYOUT OF CMOS INVERTER TAKEN USING MAGIC VLSI OPENSOURCE TOOL:

